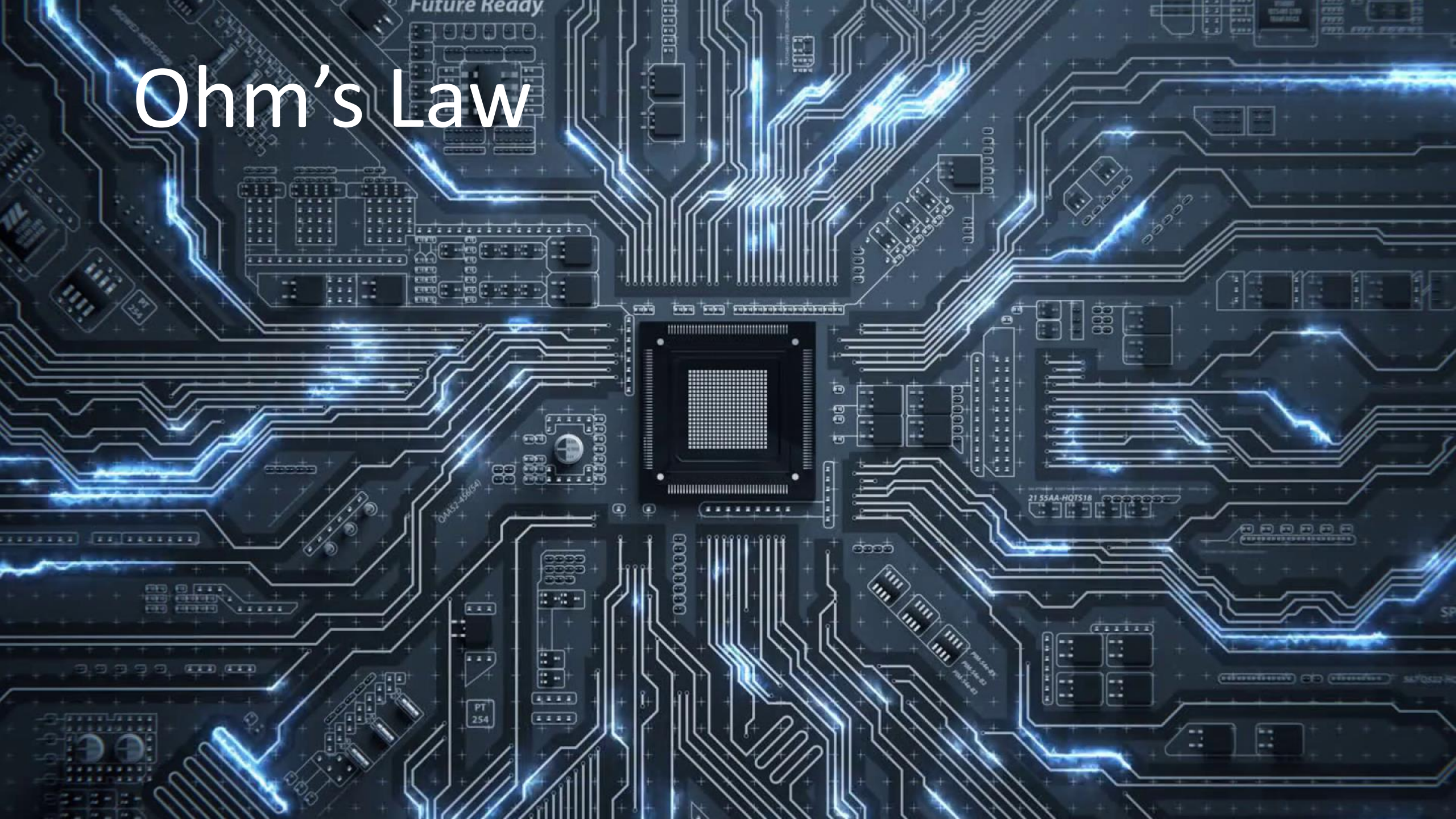


Circuits

The background is a complex, high-tech circuit board. It features a dense network of glowing blue lines representing electrical traces. Various electronic components are visible, including integrated circuits (chips) with labels like 'PT 254', '21 55AA-HQTS18', and 'QAA52-486(4)'. There are also capacitors, resistors, and other small components scattered across the board. The overall aesthetic is futuristic and digital, with a dark blue background and bright blue highlights from the glowing traces.

Engr Ghulam Raza

Ohm's Law



Ohm's Law

Current

- Rate of flow of charge
 - Amount of charge per unit time that crosses one point

$$I = \frac{\Delta Q}{\Delta t}$$

- Symbol: (I)
- Unit: ampere (A)



Ohm's Law

- Small computer speakers often have power supplies that give 12 V at 200 mA. How much charge flows through the circuit in 1 hour and how much energy is used to deliver this charge?
- $\Delta Q = 720 \text{ C}$
- $E = 8640 \text{ J}$

Ohm's Law

Conventional Current

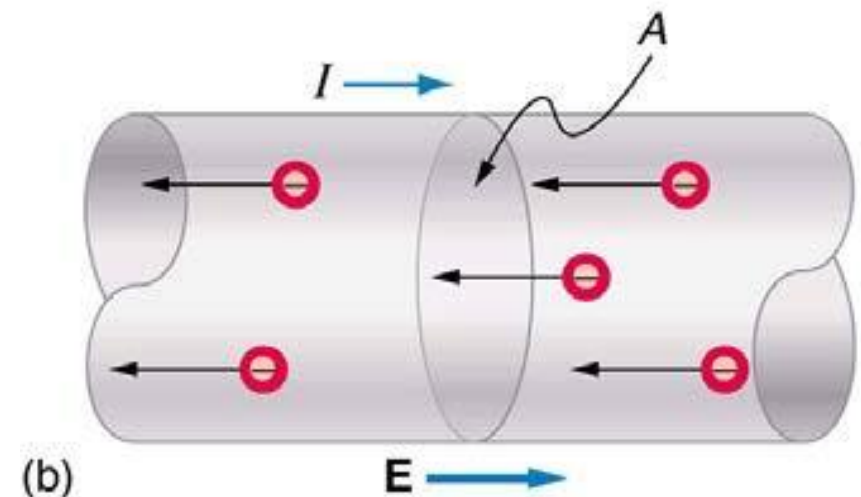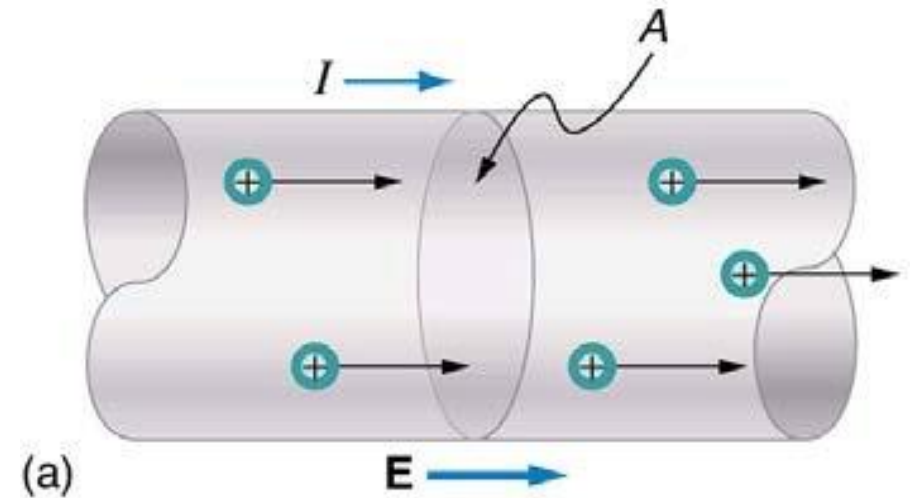
- Electrons are the charge that flows through wires
- Historically thought positive charges move
- Conventional current → imaginary flow of positive charges
 - Flows from positive terminal and into negative terminal
 - Real current flows the opposite way



Ohm's Law

Drift Velocity

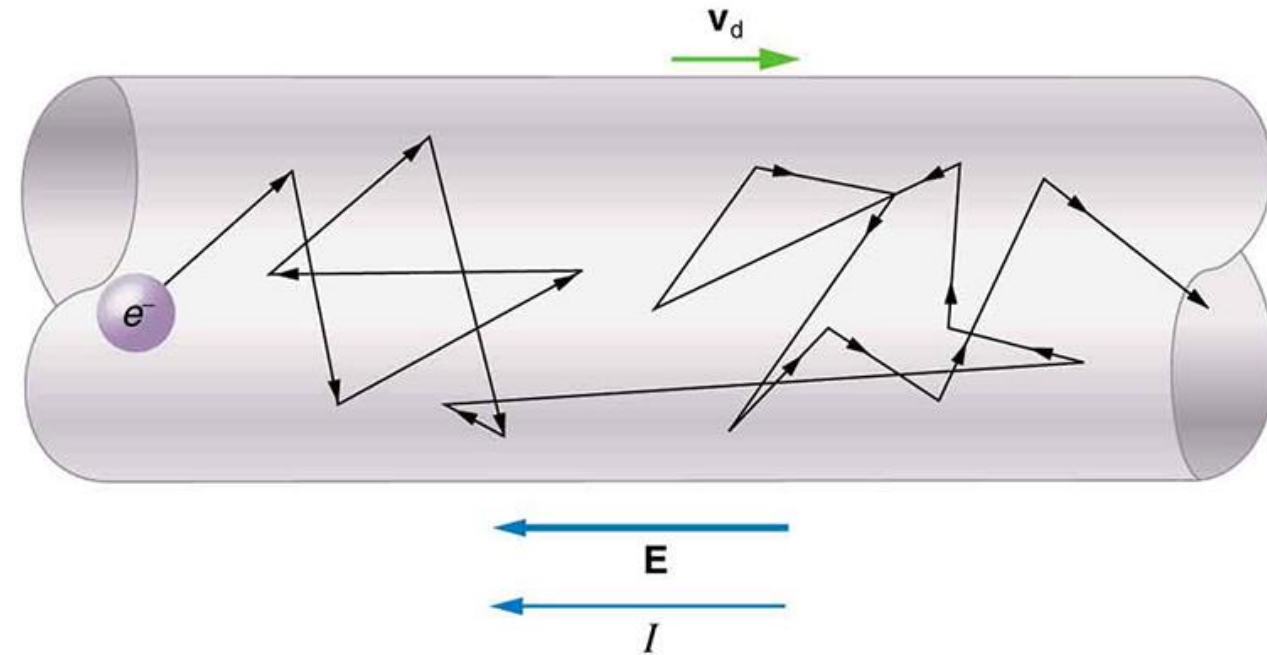- Electrical signals travel near speed of light, but electrons travel much slower
- Each new electron pushes one ahead of it, so current is actually like wave
- $I = \frac{\Delta Q}{\Delta t} = \frac{qnAx}{\Delta t} = qnAv_d$
 - q = charge of each electron
 - n = free charge density
 - A = cross-sectional area
 - v_d = drift velocity



Ohm's Law

- Think of water pumps
 - Bigger pumps → more water flowing
 - Skinny pipes (more resistance) → less water flow
- Electrical Circuits
 - Bigger battery voltage → more current
 - Big electrical resistance → less current

Ohm's Law

Ohm's Law


$$I = \frac{V}{R} \text{ or } V = IR$$

- V = emf
- I = current
- R = resistance
 - Unit: $V/A = \text{ohm } (\Omega)$

Ohm's Law

Resistors

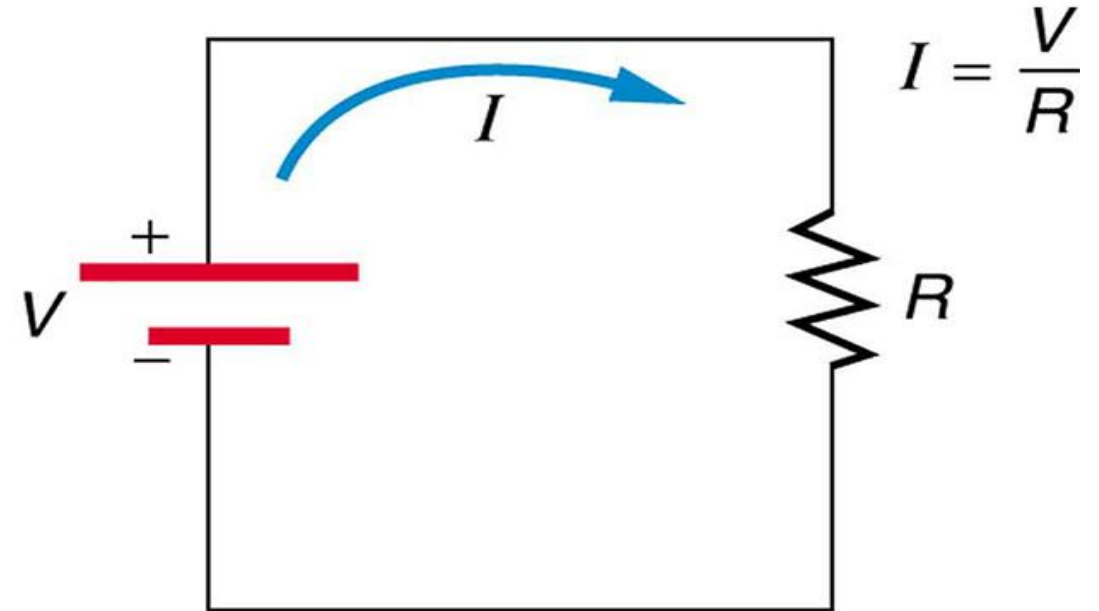
- Device that offers resistance to flow of charges
- Copper wire has very little resistance
- Symbols used for
 - Resistor →
 - Wire →



Ohm's Law

- Our speakers use 200 mA of current at maximum volume. The voltage is 12V. The current is used to produce a magnet which is used to move the speaker cone. Find the resistance of the electromagnet.
- $R = 60 \, \Omega$

Series Circuits

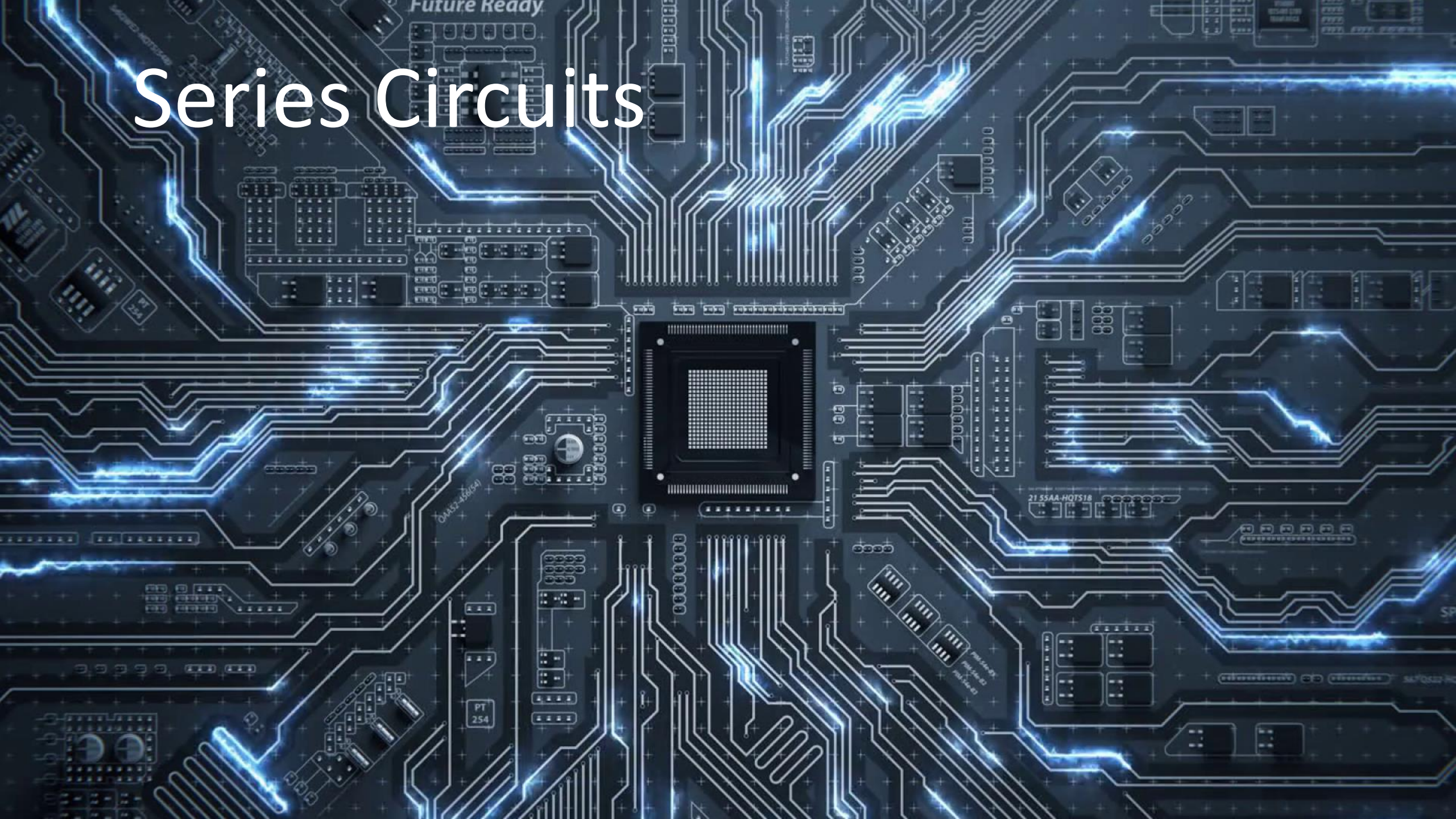


Series Circuits


Electric circuit

- Must be a complete loop
- The electric potential at battery is high
- The electric charges flow (current) down to the low potential
- Along the way, the electric potential energy is used by the devices on the circuit
- When the charges reach the low potential, there is no potential left. It has all been used.
- Without a complete loop, there is no low potential for the charges to be attracted to

Series Circuits

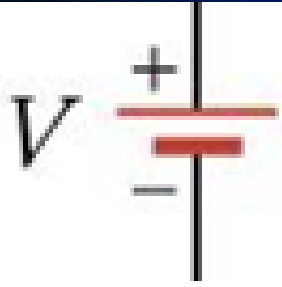

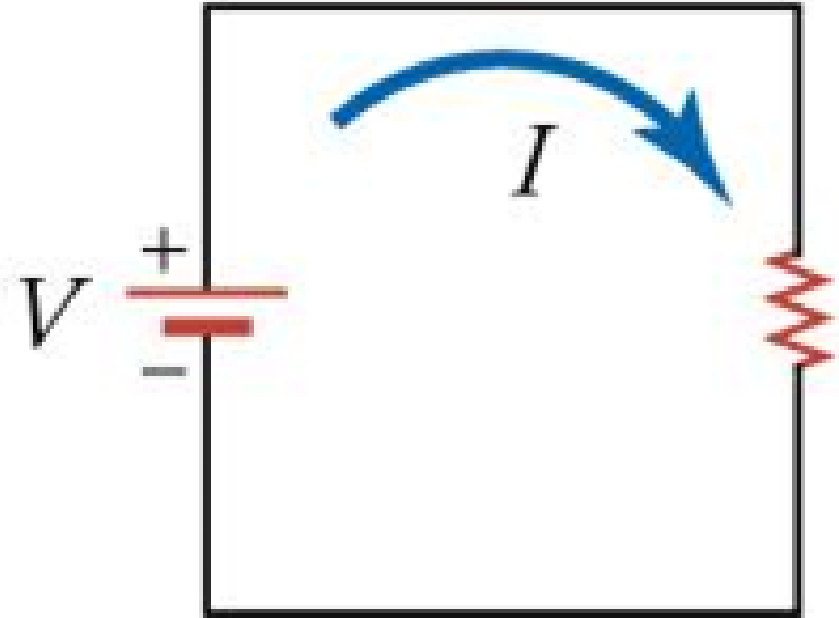
- Battery: Long side is positive, short side is negative
- Provides the potential to make the current flow
- Current flows from positive side to negative side
- Resistor: Uses the potential to do work



Series Circuits

Series Wiring

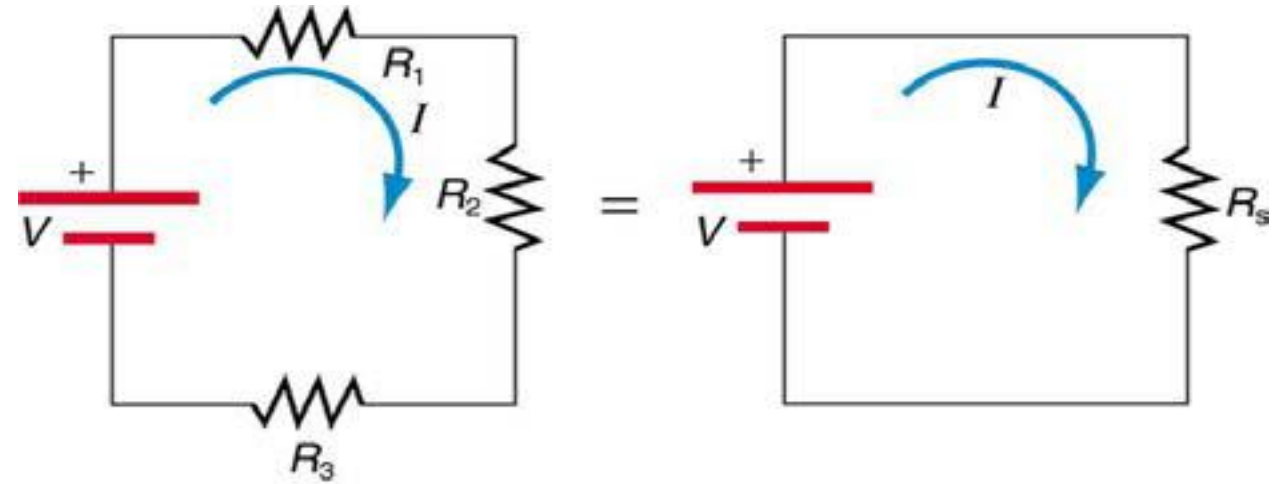- More than one device on circuit
- Same current through each device
- Break in device means no current
- Form one “loop”
- The resistors divide the voltage between them



Series Circuits

- V divide among resistors

- $V = V_1 + V_2 + V_3$


- $V = IR$

- $V = IR_1 + IR_2 + IR_3$

- $V = I(R_1 + R_2 + R_3)$


- $V = IR_S$

- $R_S = R_1 + R_2 + R_3 + \dots$

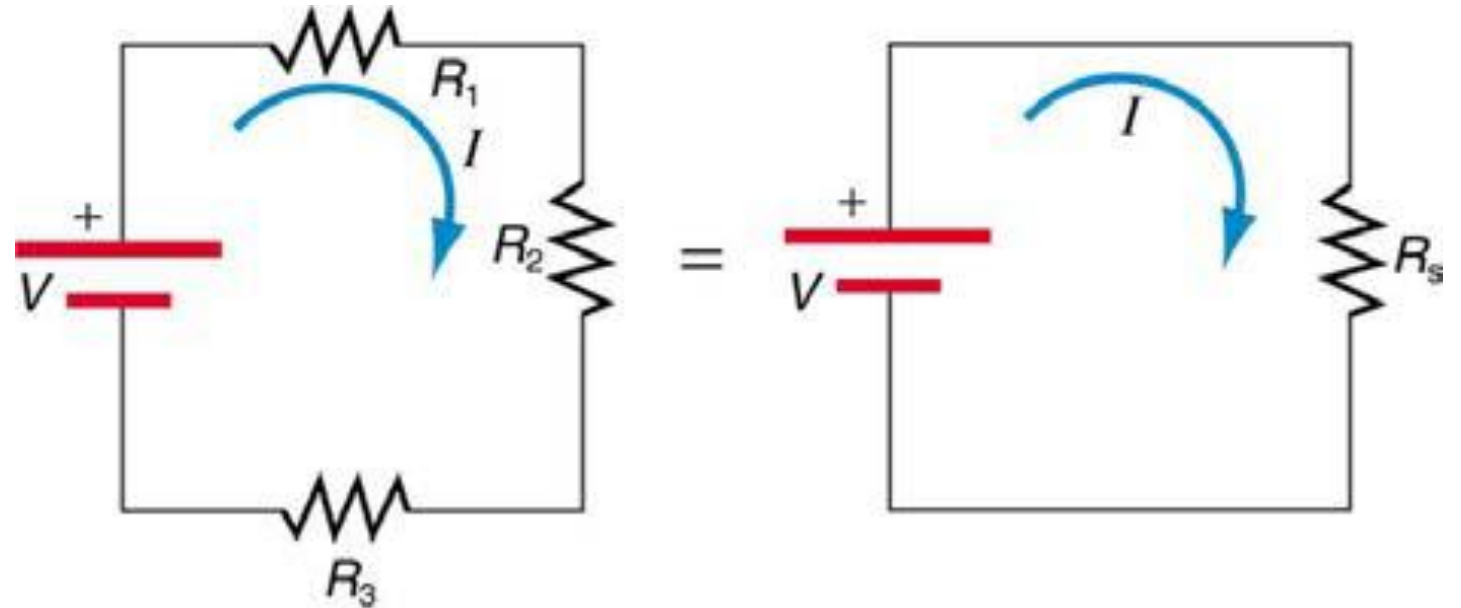

Series Circuits

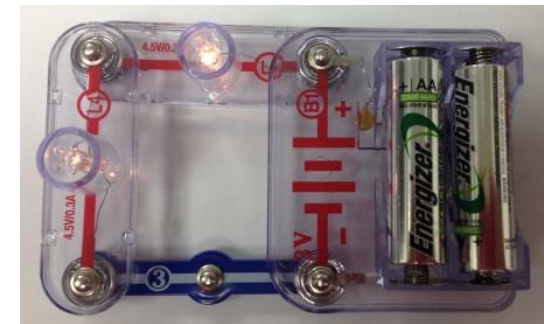- A $5.17\text{ k}\Omega$ resistor and a $10.09\text{ k}\Omega$ resistor are connected in series. What is the equivalent resistance?
- $15.26\text{ k}\Omega$




Series Circuits

- Bathroom vanity lights are occasionally wired in series. $V = 120\text{ V}$ and you install 3 bulbs with $R = 8\Omega$ and 1 bulb with $R = 12\Omega$. What is the current and voltage of each bulb?
- $I = 3.33\text{ A}$
- $V = 26.7\text{ V}, 40\text{ V}$





Parallel Circuits

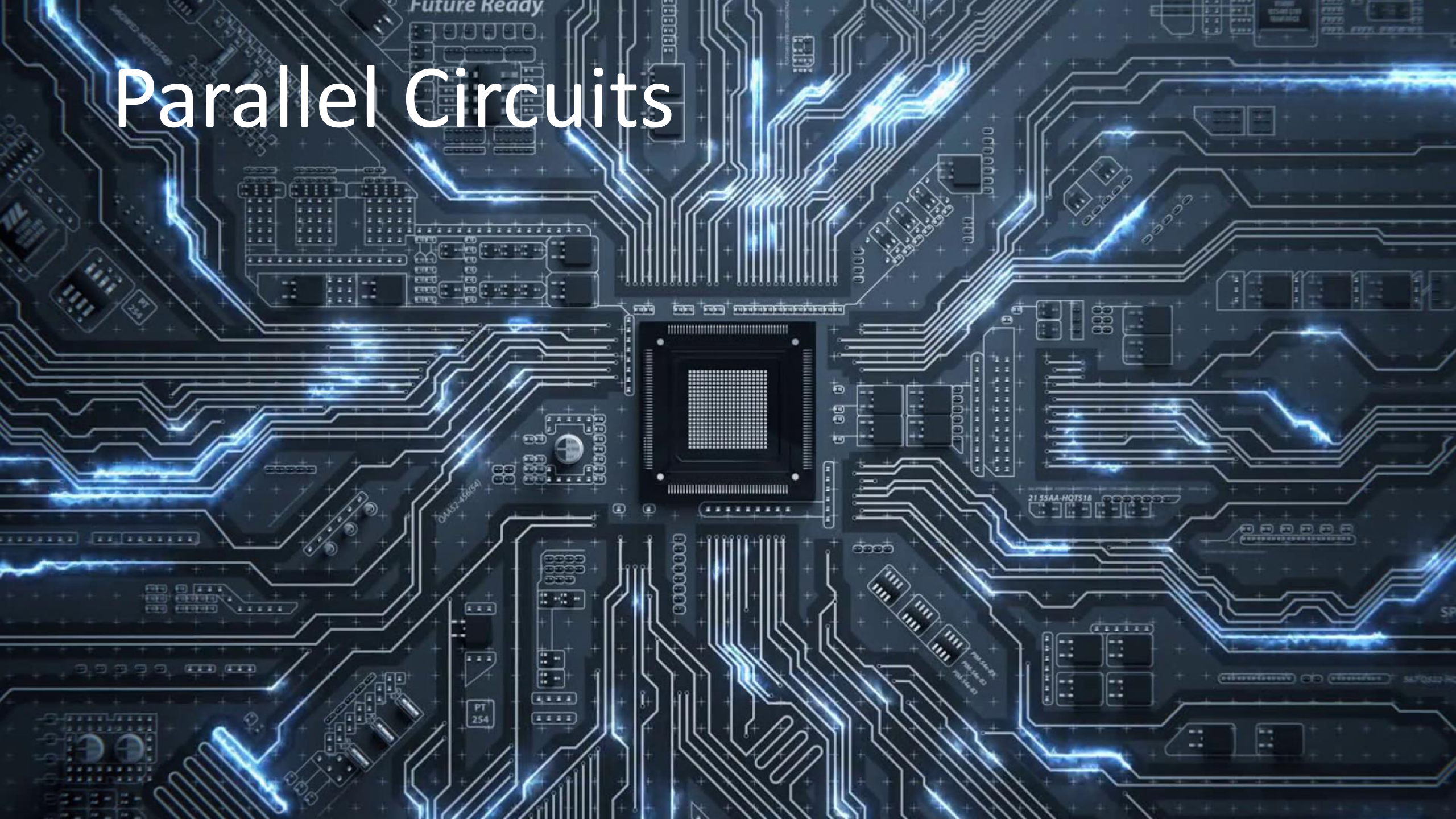

Parallel Circuit

Parallel Wiring

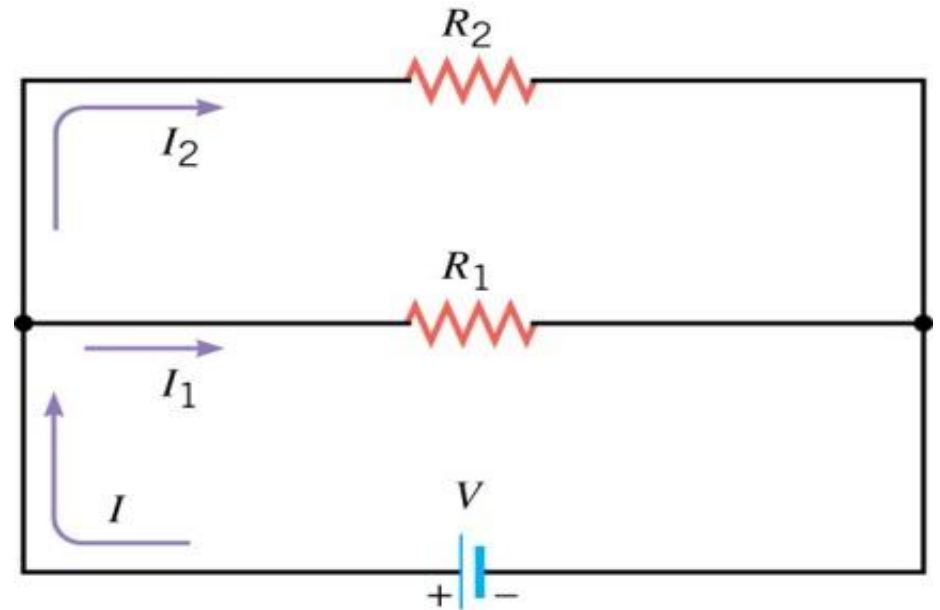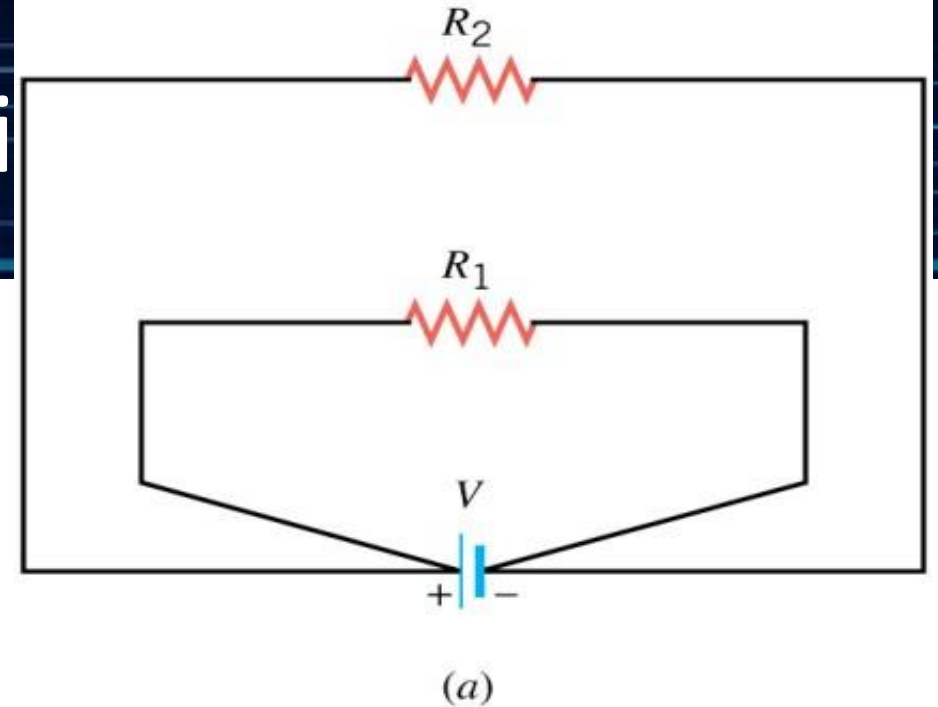
- Same voltage across several devices
- Typical house wiring
- Break in device has no effect on current
- Resistors divide current



Parallel Circuits

Derivation

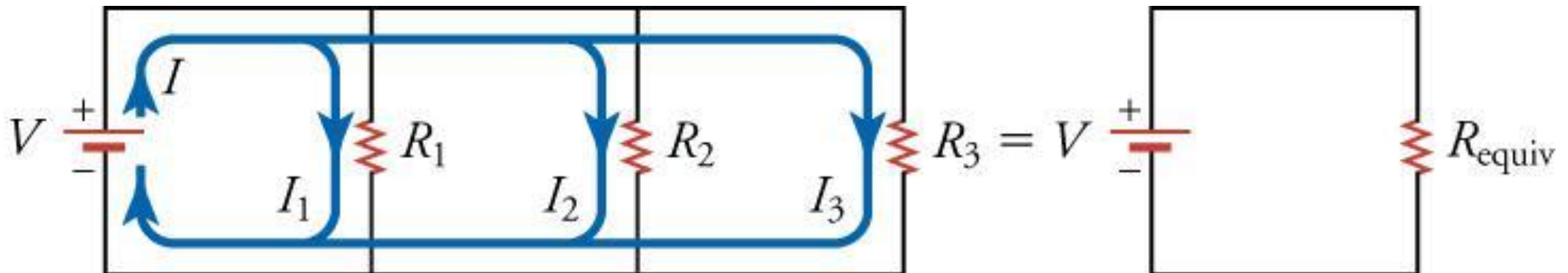- Each branch draws current as if the other wasn't there
- Each branch draws less current than the power supply gives
- $R = V / I$
- Overall circuit: Large $I \rightarrow$ Small R
 - Smaller resistance than either branch



Parallel Circuits

$$I = I_1 + I_2$$

$$I = \frac{V}{R}$$

$$I = \frac{V}{R_1} + \frac{V}{R_2}$$

$$I = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = V \left(\frac{1}{R_P} \right)$$

Parallel Circuits

Parallel Resistors


$$\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

Parallel Circuits

- A $1004\ \Omega$ resistor and a $101\ \Omega$ resistor are connected in parallel. What is the equivalent resistance?
- $91.8\ \Omega$
- If they were connected to a $3\ \text{V}$ battery, how much total current would the battery supply?
- $32.7\ \text{mA}$
- How much current through each resistor?
- $3.0\ \text{mA}$ and $29.7\ \text{mA}$



Circuits in Parallel and Series





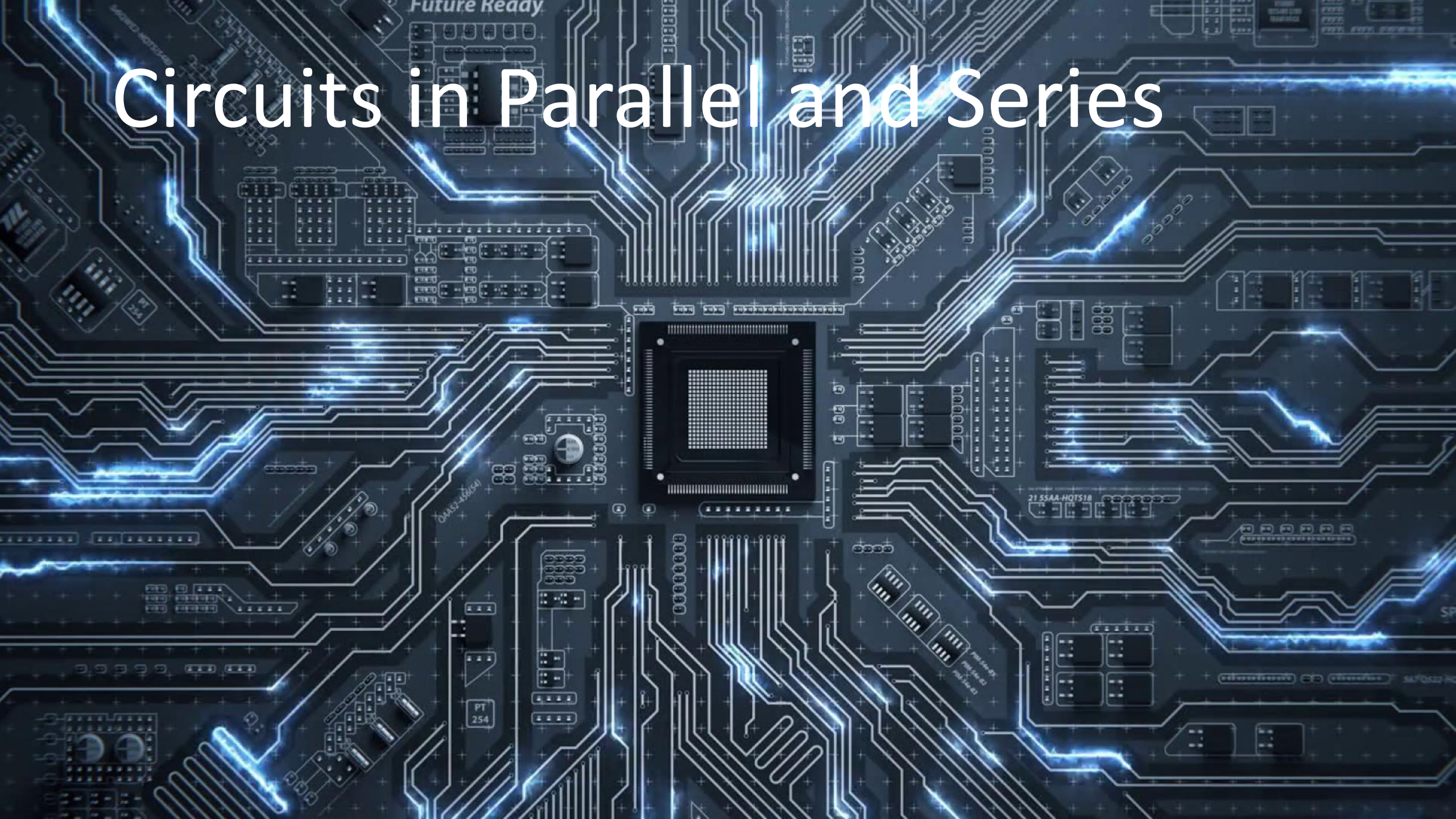


Circuits in Parallel and Series

Circuits Wired Partially in Series and Partially in Parallel


- Simplify any series portions of each branch
- Simplify the parallel circuitry of the branches
- If necessary, simplify any remaining series

Circuits in Parallel and Series

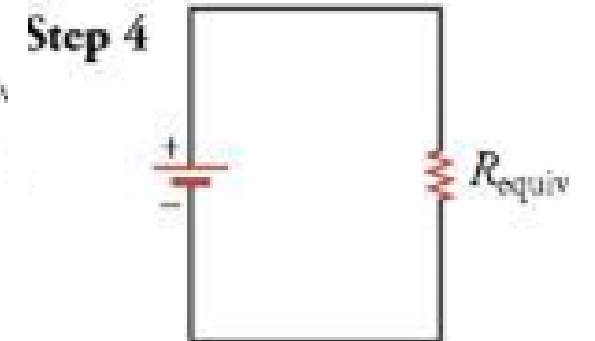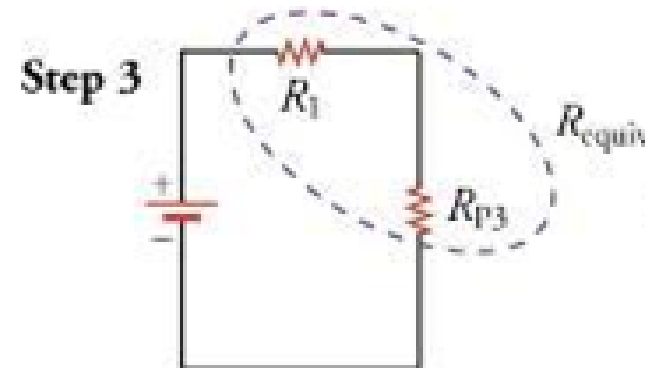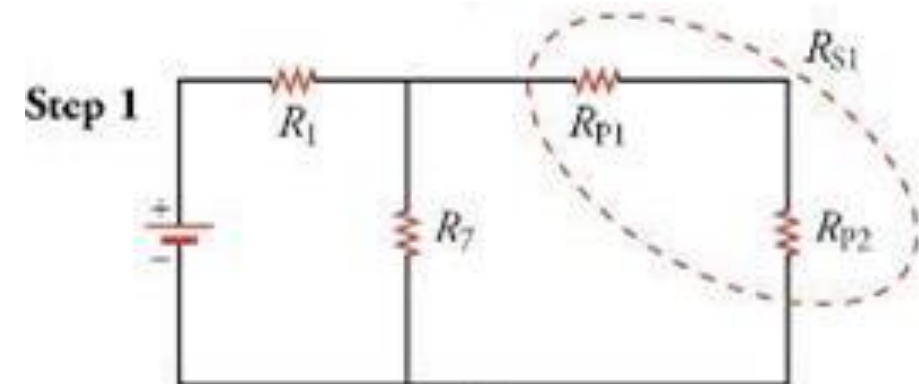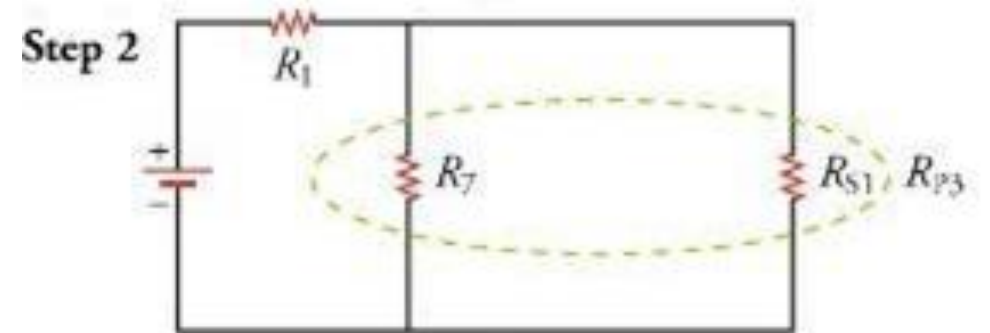
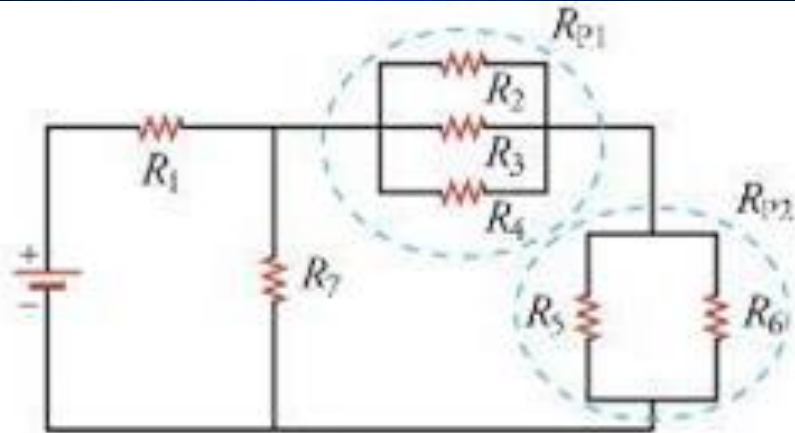


Circuits in Parallel and Series


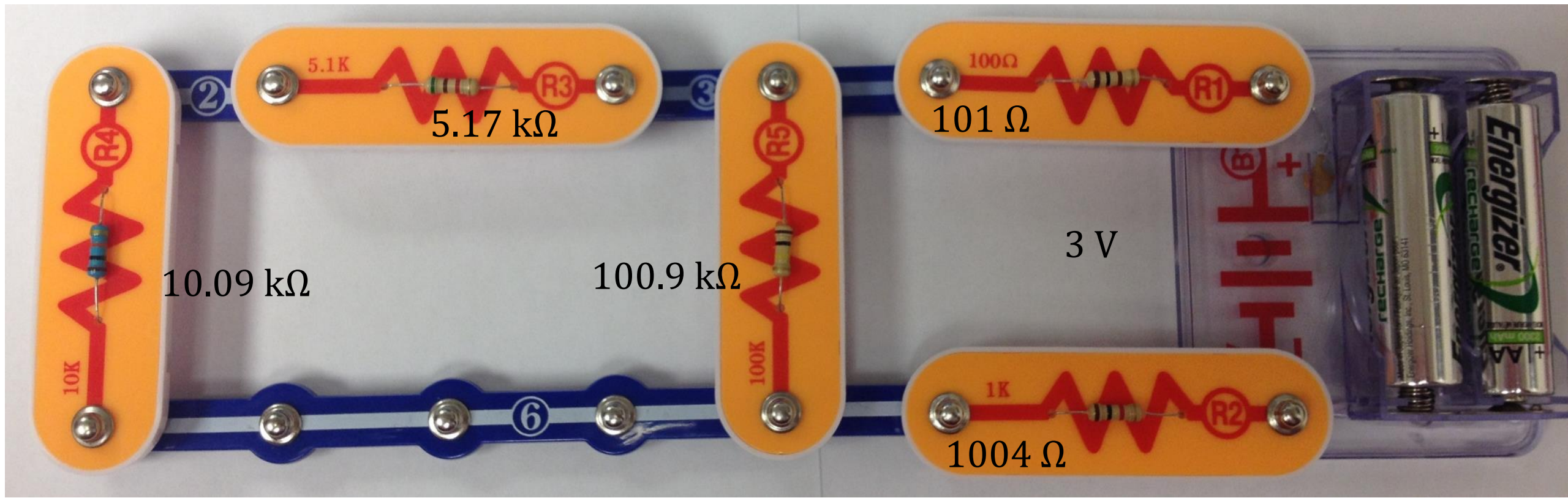
- Find the equivalent resistance and the total current of the following circuit.



Circuits in Parallel and Series

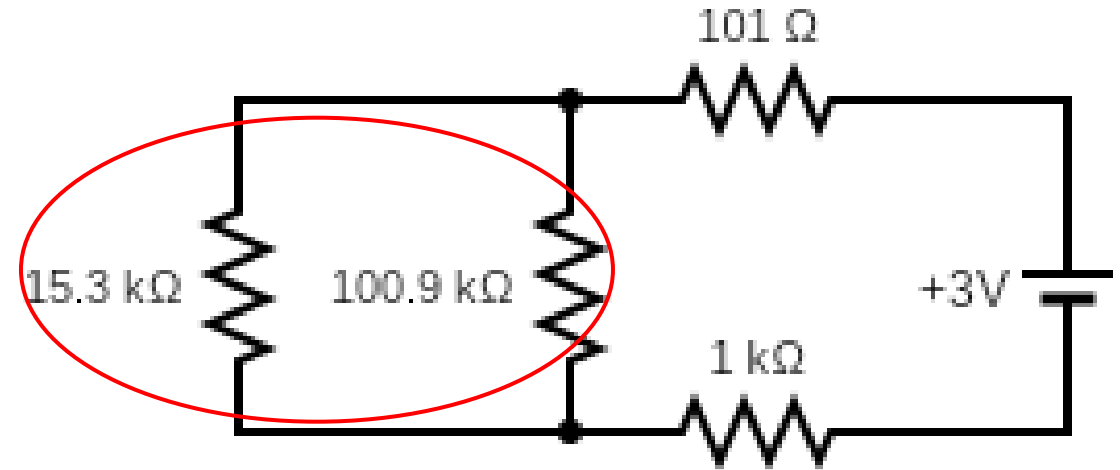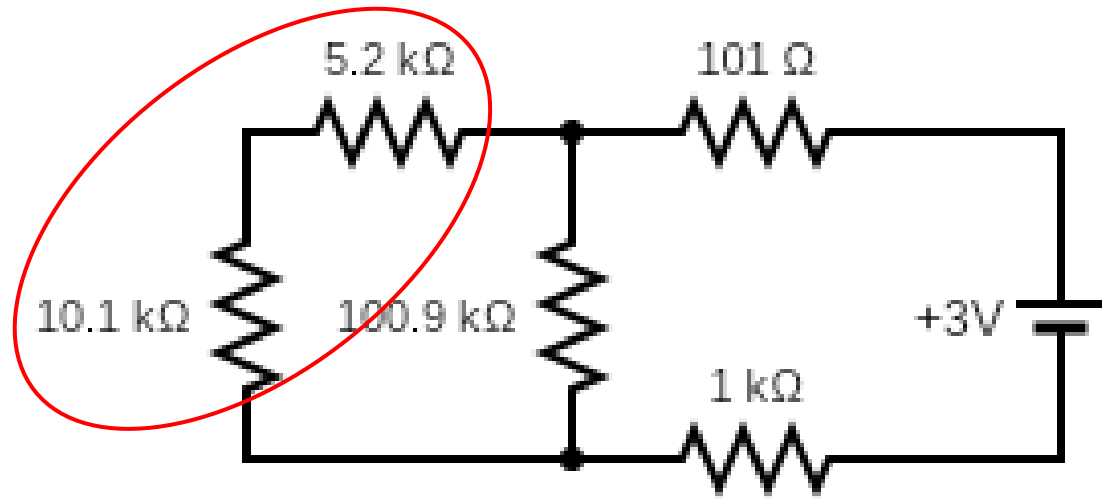


Circuits in Parallel and Series

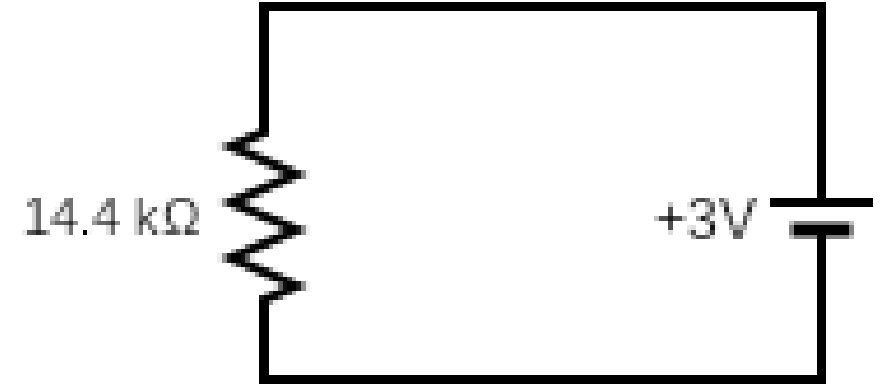
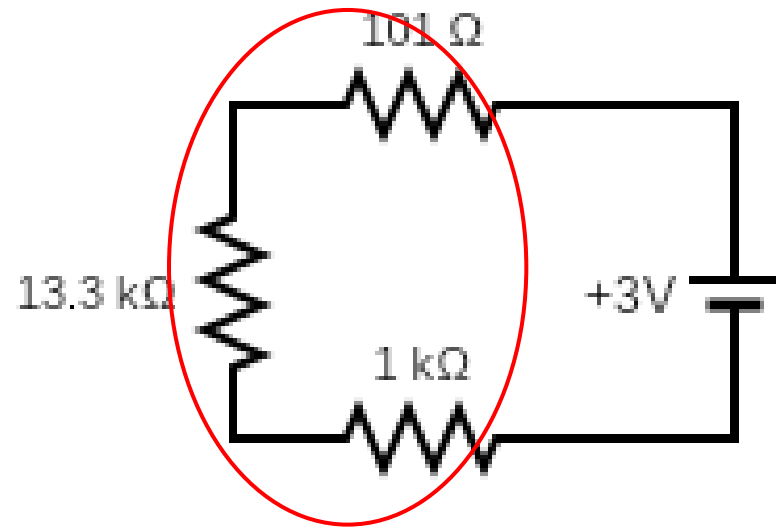


Circuits in Parallel and Series




- Find the equivalent resistance.

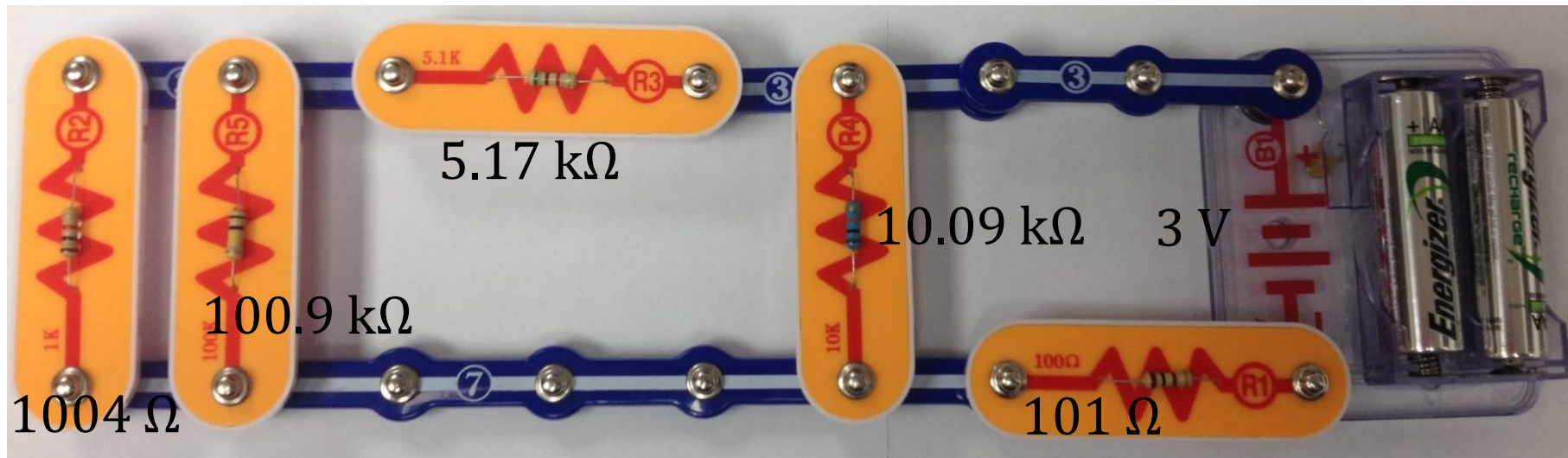


Circuits in Parallel and Series

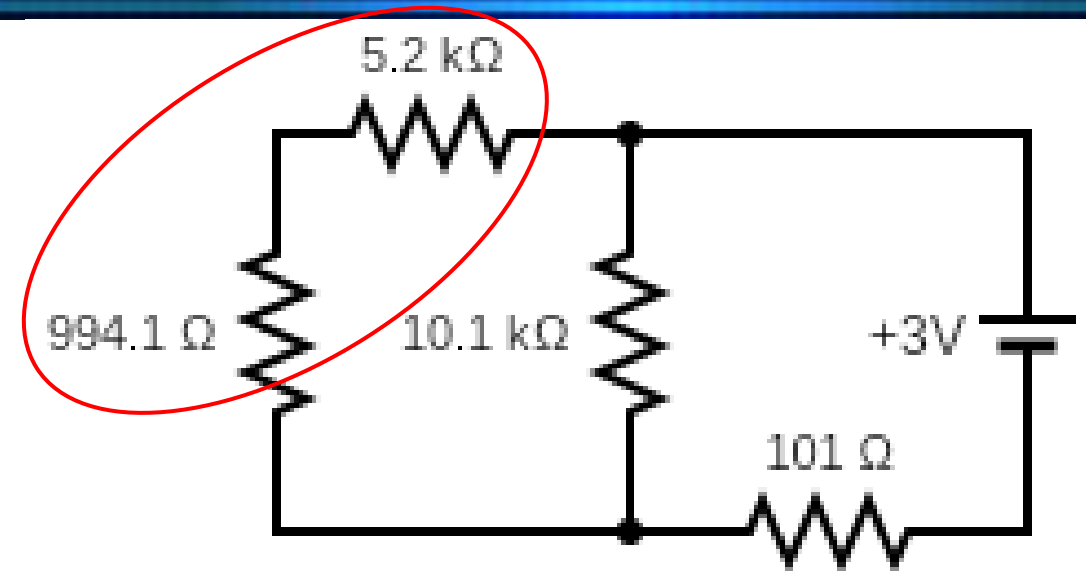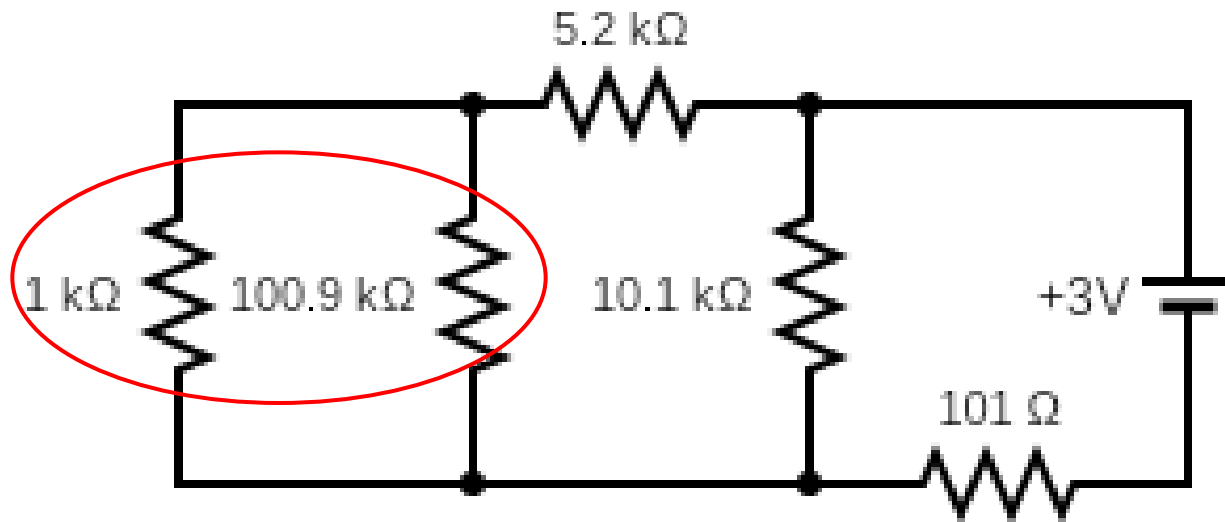

Circuits in Parallel and Series

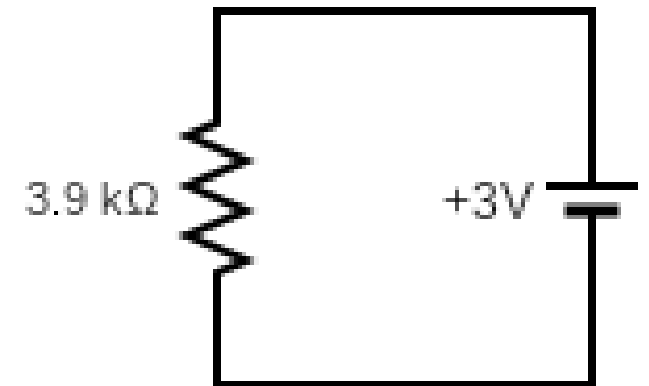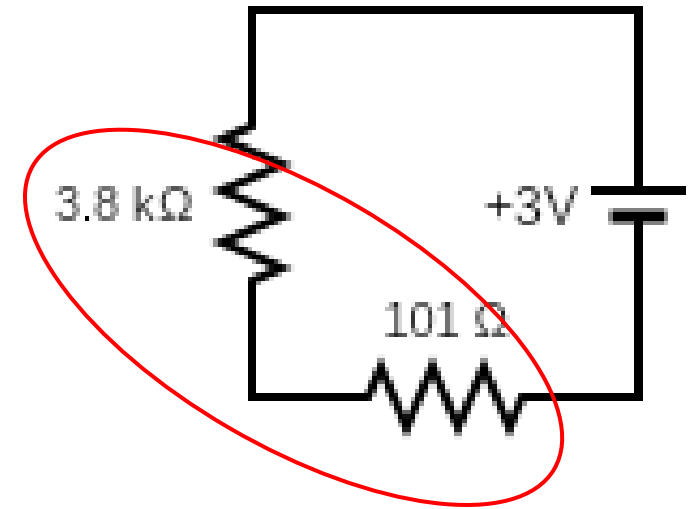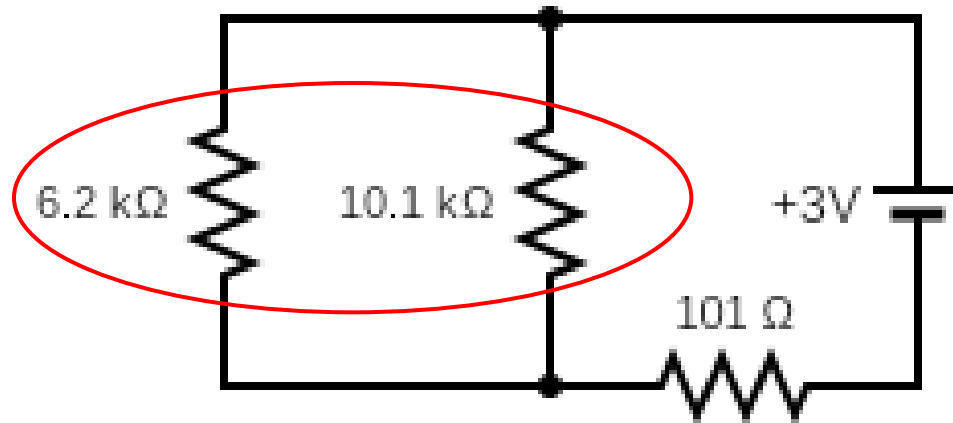


Voltmeters and Ammeters

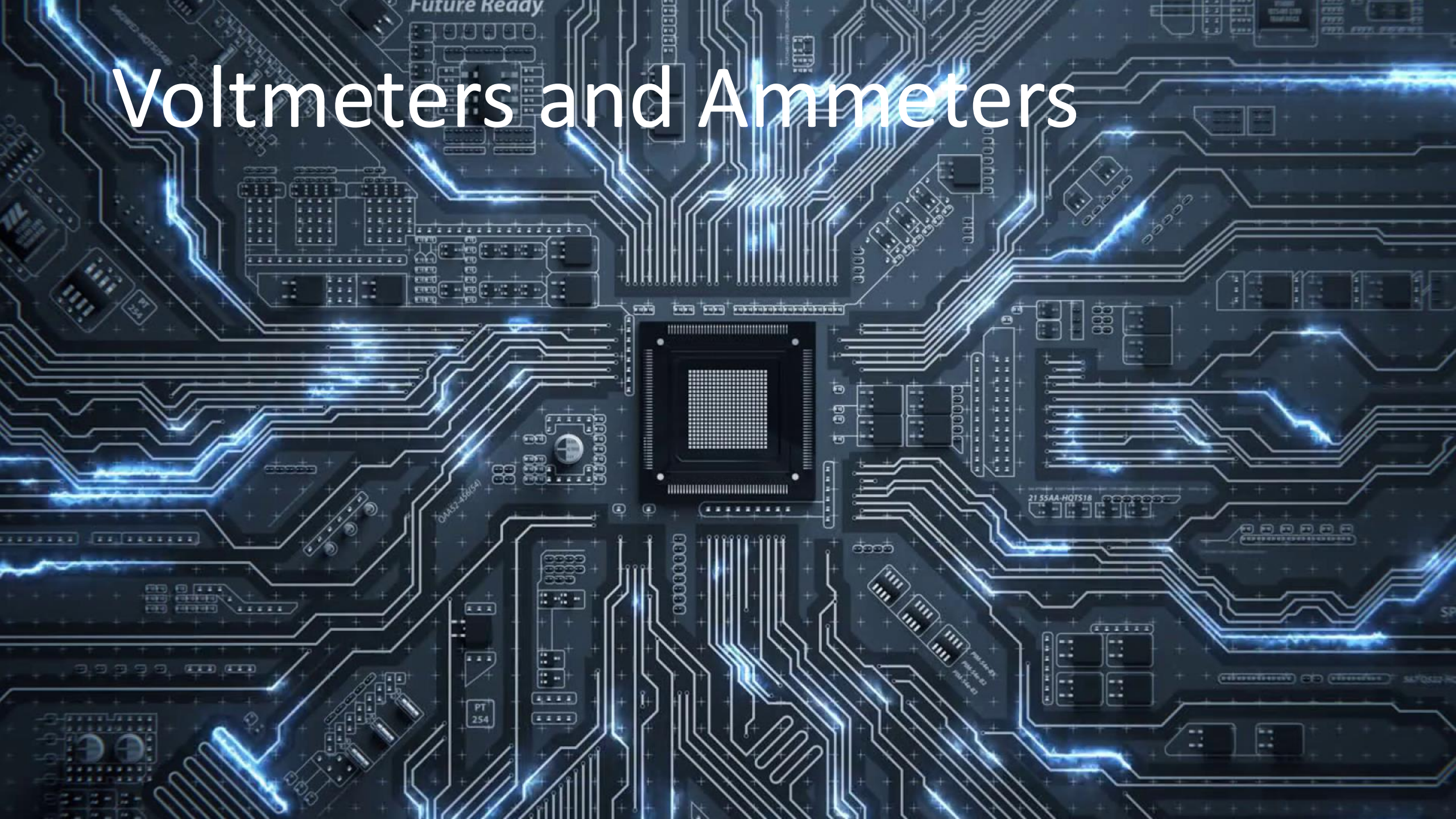

Voltmeters and Ammeters

- Analog (non-digital) meters

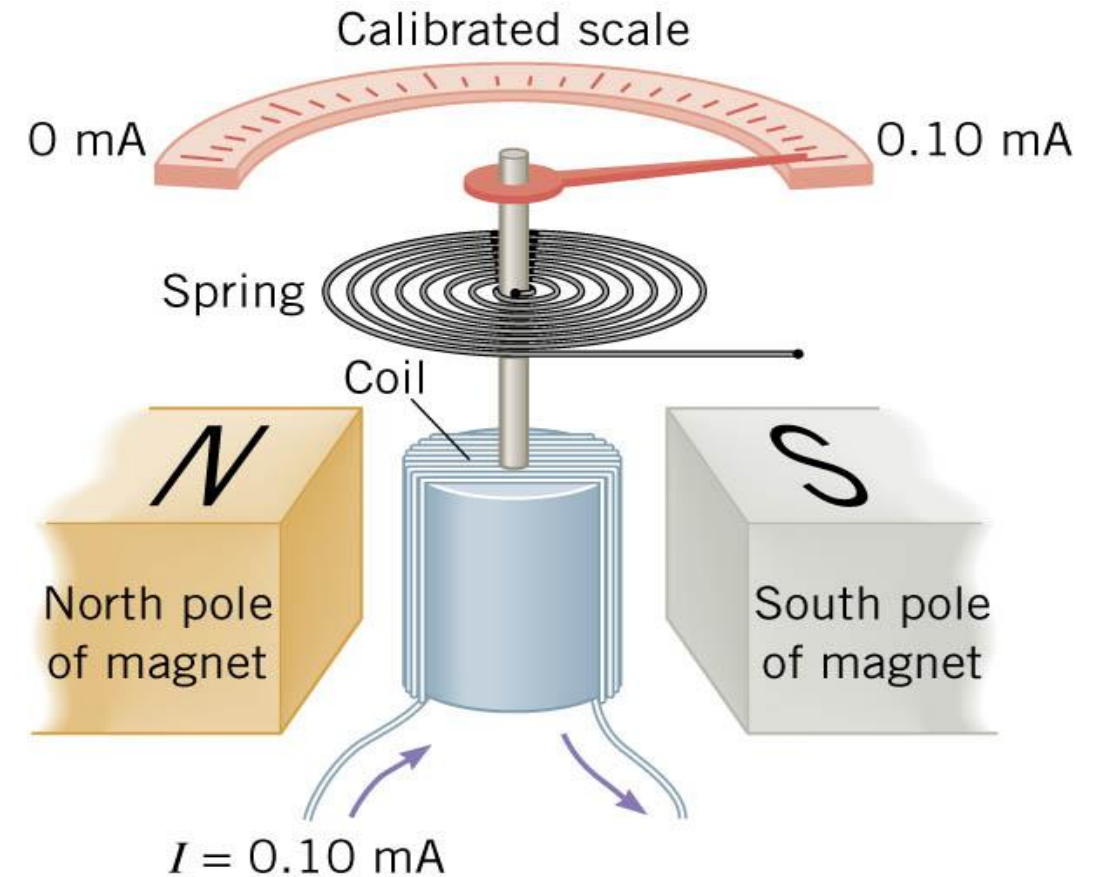

Voltmeters and Ammeters


Ammeters

- Measures current
- Inserted into circuit so current passes through it
 - Connected in series



Voltmeters and Ammeters

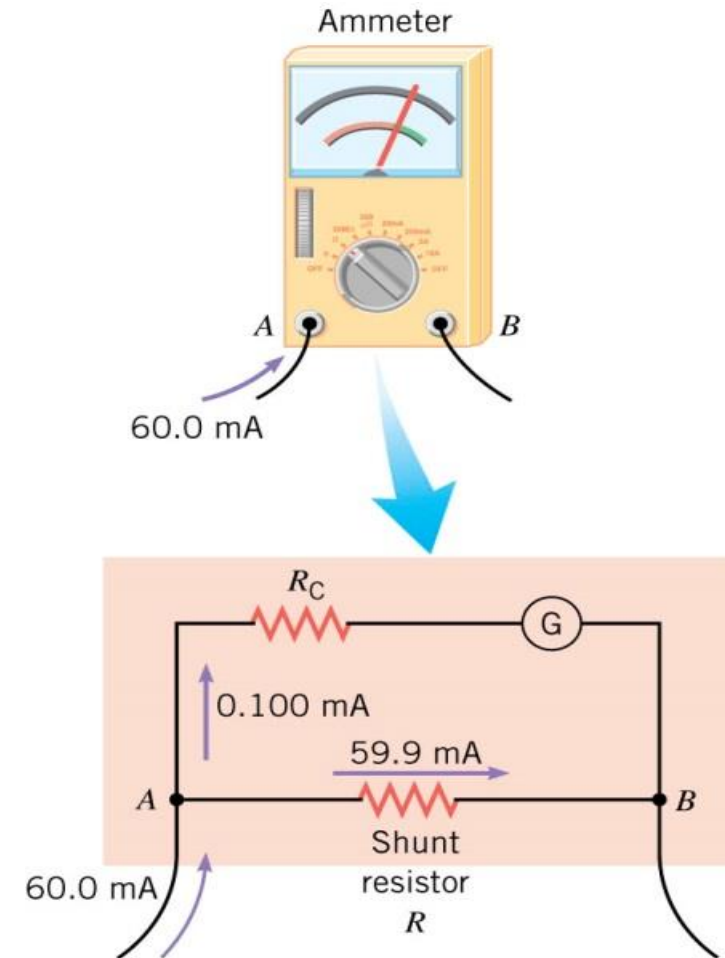- Coil usually measures only little current
- Has shunt resistors connected in parallel to galvanometer so excess current can bypass
 - A knob lets you select which shunt resistor is used




Voltmeters and Ammeters

- Problems with Ammeters
 - The resistance of the coil and shunt resistors add to the resistance of the circuit
 - This reduces the current in the circuit
 - Ideal ammeter has no resistance
 - Real-life good ammeters have small resistance so as only cause a negligible change in current

Voltmeters and Ammeters

Voltmeters

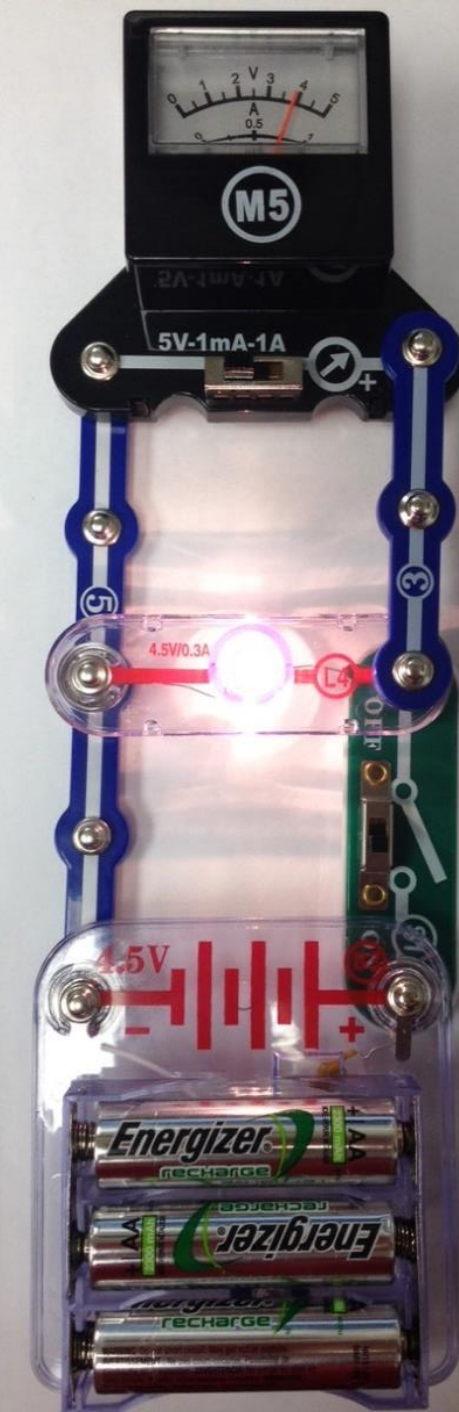
- Connected in parallel to circuit since parallel has same voltage
- The coil works just like in the ammeter
- Given the current and the resistance of the coil $\rightarrow V = IR$
- To give more range, a large resistor is connected in series with the coil



Voltmeters and Ammeters

- Problems with Voltmeters
 - The voltmeter takes some the voltage out of the circuit
 - Ideal voltmeter would have infinitely large resistance as to draw tiny current
 - Good voltmeter has large enough resistance as to make the current draw (and voltage drop) negligible

Electric Power and AC/DC Currents

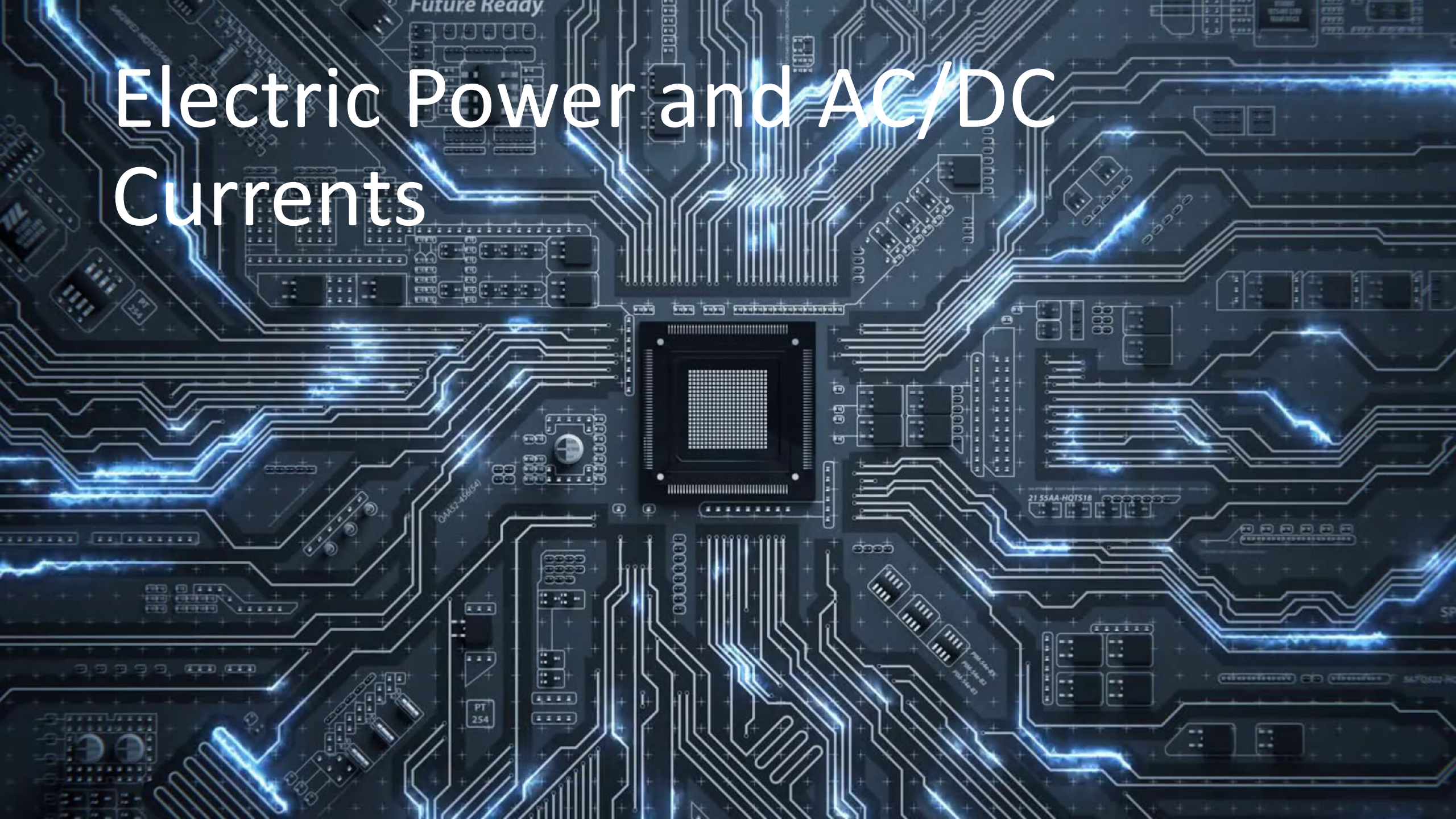The background is a high-resolution image of a circuit board. It features a complex network of white and blue traces on a dark blue background. Several components are visible, including a central square chip with a grid of pins, various rectangular integrated circuits, and smaller surface-mount components. Some components are labeled with text like "PT 254", "21 55AA-HQTS18", and "QW452-488(64)". The entire board is illuminated with a vibrant blue glow, with some areas appearing to have a lightning-bolt-like effect, suggesting high energy or power flow.

Electric Power and AC/DC Currents

$$P = \frac{W}{t}$$

$$W = \Delta E_{PE} = (\Delta q)V$$

$$P = \frac{(\Delta q)V}{t}$$

$$I = \frac{\Delta q}{t}$$

$$P = IV$$

Electric Power and AC/DC Currents

Power

$$P = IV$$

- Unit: Watt (W)
- Other equations for electrical power
 - $P = I(IR) = I^2 R$
 - $P = \left(\frac{V}{R}\right) V = \frac{V^2}{R}$

Electric Power and AC/DC Currents

- Let's say an electric heater has a resistance of $1430\ \Omega$ and operates at 120V . What is the power rating of the heater? How much electrical energy does it use in 24 hours?
- $P = 10.1\ \text{W}$
- $E = 873\ \text{kJ}$

Electric Power and AC/DC Currents


Kilowatt hours

- Electrical companies charge you for the amount of electrical energy you use
- Measured in kilowatt hours (kWh)
- If electricity costs \$0.15 per kWh how much does it cost to operate the previous heater ($P = 10.1 \text{ W}$) for one month?
- \$1.09

Electric Power and AC/DC Currents

Alternating Current

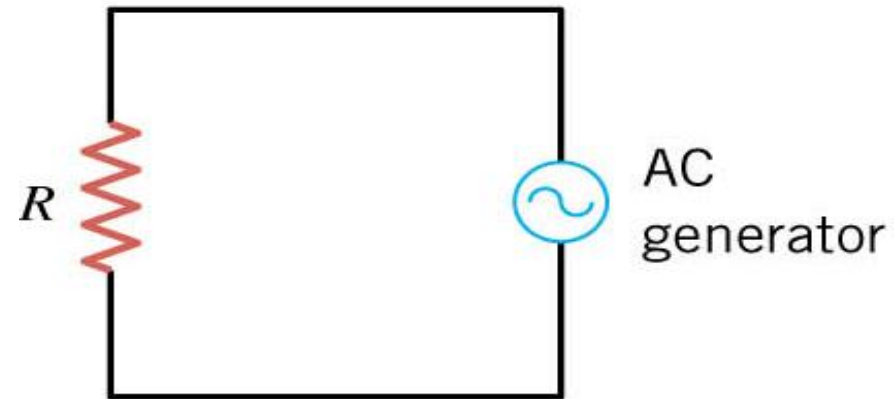
- Charge flow reverses direction periodically
- Due to way that power plants generate power
- Simple circuit



Electric Power and AC/DC Currents

Periodicity

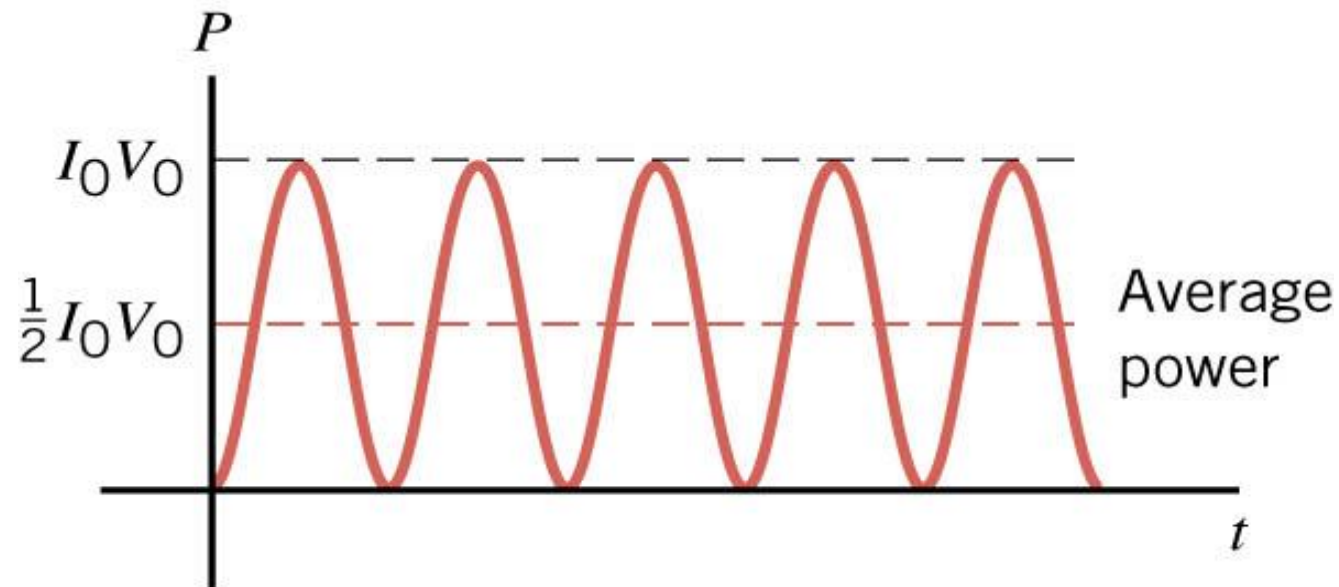- Voltage, Current, and Power fluctuate with time



- So we usually talk about the averages

Electric Power and AC/DC Currents

Average Power

- DC
 - $P = IV$
- AC
 - $P_{max} = I_0 V_0$
 - $P_{min} = 0$
 - $P_{ave} = \frac{1}{2} I_0 V_0$
- Often P is used to represent average power in all AC circuits.

Electric Power and AC/DC Currents

Root Mean Square (rms)

$$P_{ave} = \frac{1}{2} I_0 V_0 = \left(\frac{I_0}{\sqrt{2}} \right) \left(\frac{V_0}{\sqrt{2}} \right) = I_{rms} V_{rms}$$

- I_{rms} and V_{rms} are called root mean square current and voltage
- Found by dividing the max by $\sqrt{2}$

$$I_{rms} = \frac{I_0}{\sqrt{2}}$$

$$V_{rms} = \frac{V_0}{\sqrt{2}}$$


Electric Power and AC/DC Currents

- A 60 W light bulb operates on a peak voltage of 156 V. Find the V_{rms} , I_{rms} , and resistance of the light bulb.
- $V_{rms} = 110 \text{ V}$
- $I_{rms} = 0.55 \text{ A}$
- $R = 202 \text{ } \Omega$

Electric Power and AC/DC Currents

- Why are you not supposed to use extension cords for devices that use a lot of power like electric heaters?
- $P = IV$
 - P is large so I is large
- The wire has some resistance
- The large current and little resistance can cause heating
- If wire gets too hot, the plastic insulation melts

Electricity and the Human Body

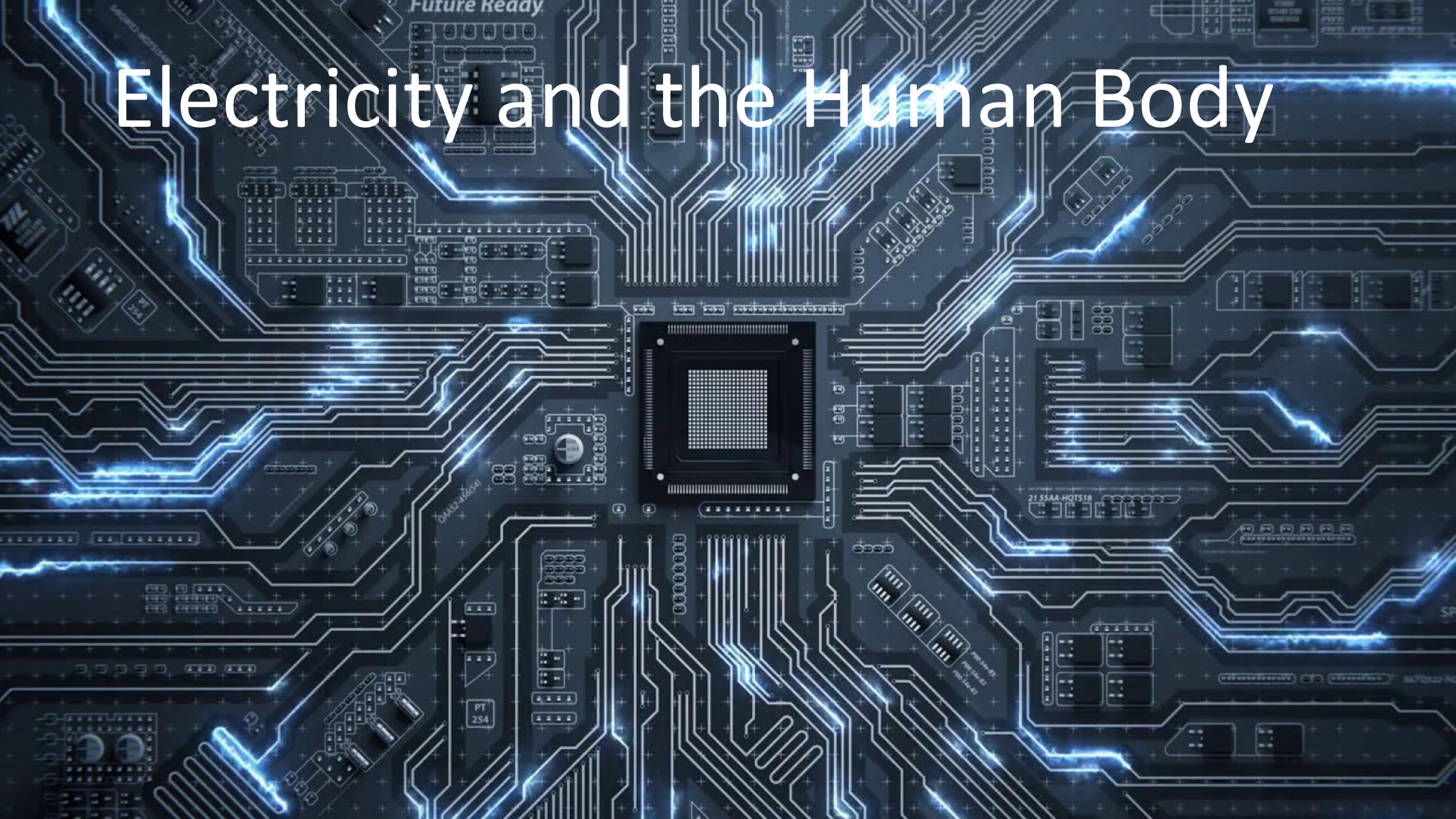

Electricity and the Human Body

- Thermal Hazards
 - Electric energy converted to thermal energy faster than can be dissipated
 - Happens in short circuits
 - Electricity jumps between two parts of circuits bypassing the main load
- $P = \frac{V^2}{R}$
 - Low R so high P
 - Can start fires
 - Circuit breakers or fuses try to stop
- Or long wires that have
 - High resistance (thin)
 - Or are coiled so heat can't dissipate

Electricity and the Human Body

- Shock Hazards
 - Factors
 - Amount of Current
 - Path of current
 - Duration of shock
 - Frequency of current
- Human body mainly water, so decent conductor
- Muscles are controlled by electrical impulses in nerves
- A shock can cause muscles to contract
 - Cause fist to close around wire (muscles to close, stronger than to open)
- Can cause heart to stop
- Body most sensitive to 50-60 Hz